QUESTION ANALYSIS

EEE337

Power System II

Question Analysis

Sessions 2020–21 to 2021–22 *2 papers, 51 questions, 96 formulas*

INSIDE

• At a glance • Heat map • Priority list • 9 topic pages • Derivations • Repeats • Styles • Study order

Prepared by Nur Mohammad

October 2026

Contents

1 At a glance **3**

2 Heat map **3**

3 Priority list **4**

4 Topic pages **4**

4.1 Line inductance 4
4.2 Line capacitance 7
4.3 Corona 8
4.4 Overhead insulators 9
4.5 Mechanical design 10
4.6 Underground cables 11
4.7 Cable faults 13
4.8 Power system stability 14
4.9 HVDC and FACTS 16

5 Derivations **16**

6 Repeat tracker **17**

7 Question style **17**

8 Study order **17**

Free shared copy · Nur Mohammad

1. At a glance:

This analysis covers **2 papers** (2020-21, 2021-22), with 51 questions and 325 marks offered. It shows what past papers asked. It does not predict the next paper, and with so few papers a pattern can easily be chance.

The five topics with the most marks:

Topic	Marks	Share	Questions	Top subtopics (marks)
Underground cables	85	26 %	11	Dielectric stress (43); Grading (20); Capacitance (10)
Line inductance	66	20 %	11	Mutual inductance (25); Composite conductors (18); Transposition (12)
Overhead insulators	48	15 %	7	String efficiency (41); Failure (7)
Power system stability	43	13 %	5	Equal area criterion (23); Transient EMF (20)
Line capacitance	27	8 %	5	Unsymmetrical spacing (25); Effect of earth (2)

A formula name in bold is a key formula.

2. Heat map:

Marks offered, by topic and paper, in book order. A darker cell means more marks. Click a topic to open its page.

Topic and subtopic	2020-21	2021-22	Term tests	All
Line inductance	**30**	**26**	**10**	**66**
Mutual inductance	**10**	**10**	**5**	25
Composite conductors	**10**	**8**	·	18
Transposition	**4**	**8**	·	12
Bundled conductors	**4**	·	**5**	9
Basics	**1**	·	·	1
Skin effect	**1**	·	·	1
Line capacitance	**10**	**17**	·	**27**
Unsymmetrical spacing	**10**	**15**	·	25
Effect of earth	·	**2**	·	2
Corona	**6**	**2**	·	**8**
Critical disruptive voltage	**5**	**2**	·	7
Corona effect	**1**	·	·	1
Overhead insulators	**15**	**28**	**5**	**48**
String efficiency	**10**	**26**	**5**	41
Failure	**5**	**2**	·	7
Mechanical design	**10**	**7**	·	**17**
Sag	**10**	**2**	·	12
Supports	·	**5**	·	5
Underground cables	**40**	**40**	**5**	**85**
Dielectric stress	**30**	**8**	**5**	43
Grading	·	**20**	·	20
Capacitance	**10**	·	·	10
Construction	·	**5**	·	5
Insulation resistance	·	**5**	·	5
Economical size	·	**2**	·	2
Cable faults	**10**	**5**	**5**	**20**

Topic and subtopic	2020-21	2021-22	Term tests	All
Loop tests	**10**	**5**	**5**	20
Power system stability	**25**	**18**	·	**43**
Equal area criterion	**15**	**8**	·	23
Transient EMF	**10**	**10**	·	20
HVDC and FACTS	**4**	**7**	·	**11**
HVDC	·	**7**	·	7
FACTS	**4**	·	·	4

3. Priority list:

Must know: Underground cables (85), Line inductance (66), Overhead insulators (48), Power system stability (43), Line capacitance (27), Cable faults (20), Mechanical design (17), HVDC and FACTS (11), Corona (8)

Likely: none

Less often: none

The rule: Must know means asked in every paper. Likely means asked in at least half the papers. Less often means asked in fewer than half. Numbers in brackets are marks offered, and each list runs from most marks to fewest.

4. Topic pages:

4.1. Line inductance:

66 marks, 11 questions, in 2 of 2 papers. Book: Mehta Ch. 9; Grainger Ch. 4.

Most often numerical (5 of 11). Subtopics: Basics; Bundled conductors; Mutual inductance; Transposition; Composite conductors; Skin effect.

Formulas:

Subtopic	Formula	Equation	Used in
Basics	**Inductance**	$L = \frac{\psi}{I} = \frac{N\phi}{I}$	20-21 1(a)
	Induced voltage	$e = L\frac{di}{dt}$	20-21 1(a)
Bundled conductors	Internal flux linkage	$\psi_{int} = \frac{\mu_0 I}{8\pi}$	20-21 1(b), 21-22 1(c)
	External flux linkage	$\psi_{12} = \frac{\mu_0 I}{2\pi}\ln\frac{D_2}{D_1} = 2\times10^{-7}\, I \ln\frac{D_2}{D_1}$	20-21 1(b)
	GMR of a solid conductor	$D_s = r' = r\, e^{-1/4} = 0.7788\, r$	20-21 1(b)
	Transposed 3-phase line	$L = 2\times10^{-7}\ln\frac{D_{eq}}{D_s}$ H/m	20-21 1(b)
	Equivalent spacing	$D_{eq} = \sqrt[3]{D_{ab}D_{bc}D_{ca}}$	20-21 1(b)
	Two-conductor bundle	$D_s^b = \sqrt{D_s\, d}$	20-21 1(b)

Subtopic	Formula	Equation	Used in
	Inductive reactance	$X_L = 2\pi f L$	20-21 1(b), 21-22 7(a)
	Two-conductor bundle	$D_s = \sqrt{r' d}$	21-22 7(a)
Mutual inductance	**Mutual inductance**	$M = 2 \times 10^{-7} \ln \frac{D_{P_1T_2} D_{P_2T_1}}{D_{P_1T_1} D_{P_2T_2}}$ H/m	20-21 1(d), 21-22 1(d)
	Induced voltage	$E = 2\pi f M I$	20-21 1(d), 21-22 1(d)
	Symmetrical arrangement	$M = 4 \times 10^{-7} \ln \frac{D_2}{D_1}$ H/m	21-22 1(d)
Transposition	Flux linkage in a group	$\psi_a = 2 \times 10^{-7} \left[I_a \ln \frac{1}{D_s} + I_b \ln \frac{1}{D_{ab}} + I_c \ln \frac{1}{D_{ac}} \right]$	20-21 2(b)
	Inductance	$L = \frac{\psi}{I}$	21-22 1(c)
	External flux linkage	$\psi_{12} = \frac{\mu_0 I}{2\pi} \ln \frac{D_2}{D_1}$	21-22 1(c)
	GMR of a solid conductor	$r' = r\, e^{-1/4} = 0.7788\, r$	21-22 1(c)
	Symmetrical 3-phase line	$L = 2 \times 10^{-7} \ln \frac{D}{r'}$ H/m	21-22 1(c)
	Unsymmetrical transposed line	$L = 2 \times 10^{-7} \ln \frac{D_{eq}}{r'} = 0.2 \ln \frac{D_{eq}}{r'}$ mH/km	21-22 1(c)
	Equivalent spacing	$D_{eq} = \sqrt[3]{D_{12} D_{23} D_{31}}$	21-22 1(c)
Composite conductors	**Composite conductor**	$L_X = 2 \times 10^{-7} \ln \frac{D_m}{D_{sX}}$ H/m	20-21 2(c), 21-22 4(c)
	Mutual GMD	$D_m = \sqrt[mn]{(D_{aa'} D_{ab'} \cdots D_{am}) \cdots (D_{na'} \cdots D_{nm})}$	20-21 2(c), 21-22 4(c)
	Self GMD	$D_{sX} = \sqrt[n^2]{(D_{aa} D_{ab} \cdots D_{an}) \cdots (D_{na} \cdots D_{nn})}$	20-21 2(c), 21-22 4(c)
	Strand inductance	$L_X = \frac{L_a + L_b + \cdots + L_n}{n^2}$	20-21 2(c)
	Composite line loop	$L = 2 \times 10^{-7} \ln \frac{D_m^2}{D_{sX} D_{sY}}$ H/m	20-21 2(c), 21-22 4(c)
Skin effect	Skin depth	$\delta = \frac{1}{\sqrt{\pi f \mu \sigma}}$	20-21 3(a)

Questions:

No.	Paper	Marks	Type	Question
Basics				
1	20-21 1(a)	1	theory	Define Inductance with the required expression.
Bundled conductors				
2	20-21 1(b)	4	numerical	Each conductor of the bundled-conductor line shown in Fig.1 is ACSR, 1,272,000-cmil Pheasant. Find the inductive reactance in ohms per km (and per mile) per phase for d=45cm.

Free shared copy · Nur Mohammad

No.	Paper	Marks	Type	Question
3	21-22 TT1 7(a)	5	numerical	A 500 kV line has a bundling arrangement of 2 conductors per phase as shown in the Figure 1. Compute the inductive reactance per phase of this line at 50 Hz. Each conductor carries 50% of the phase current.
Mutual inductance				
4	20-21 1(d)	10	numerical	A single phase 50Hz power line is supported on a horizontal cross-arm. The spacing between conductors is 2.5m. A telephone line is also supported on a horizontal cross-arm in the same horizontal plane as the power line. The conductors of the telephone line are of solid copper spaced 0.6m between centers. The distance between the nearest conductors of the two lines is 20m. Find the mutual inductance between the circuits and the voltage per km induced in the telephone line for 150A current flowing over the power line.
5	21-22 1(d)	10	numerical	A single-phase 50 Hz power line is supported on a horizontal cross-arm. The spacing between the conductors is 3 m. A telephone line is supported symmetrically below the power line as shown in Fig. 1. Find the mutual inductance between the two circuits and the voltage induced per kilometer in the telephone line if the current in the power line is 100 A. Assume the telephone line current to be zero.
6	21-22 TT3 9(b)	5	numerical	A single phase 50Hz power line is supported on a horizontal cross-arm. The spacing between conductors is 2.5m. A telephone line is also supported on a horizontal cross-arm in the same horizontal plane as the power line. The conductors of the telephone line are of solid copper spaced 0.6m between centers. The distance between the nearest conductors of the two lines is 20m. Find the mutual inductance between the circuits and the voltage per km induced in the telephone line for 150A current flowing over the power line.
Transposition				
7	20-21 2(b)	4	theory	Define Transposed Transmission line. Explain the reason behind Transpose.
8	21-22 1(c)	8	derivation	Define transpose transmission line. Derive the expression for the inductance of three phase transmission lines with unsymmetrical spacing.
Composite conductors				
9	20-21 2(c)	10	derivation	Derive the expression of Inductance of composite conductor lines.
10	21-22 4(c)	8	derivation	Derive the expression of inductance of composite conductor lines.
Skin effect				
11	20-21 3(a)	1	theory	Define Skin Effect.

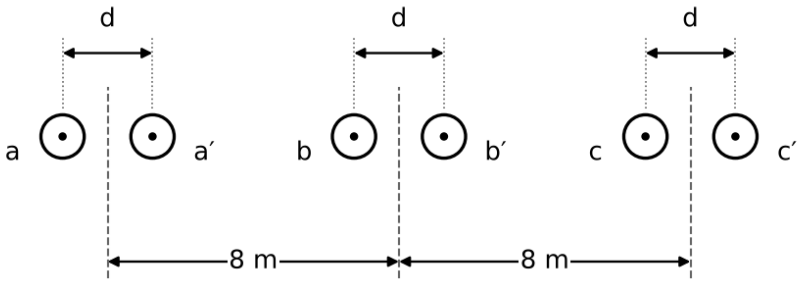


Figure 1: 20-21 1(b): Fig. 1 of the paper (redrawn): figure for Q-1(b)

Free shared copy · Nur Mohammad

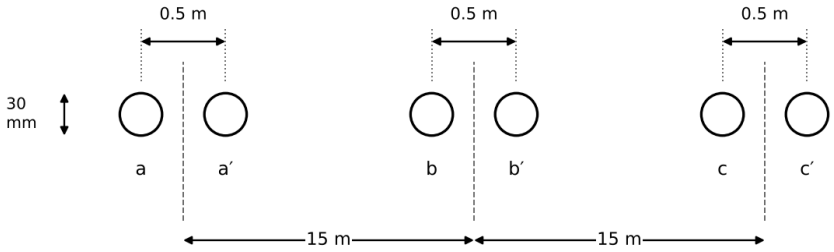


Figure 2: 21-22 TT1 7(a): Figure 1 of Term Test 1 (redrawn)

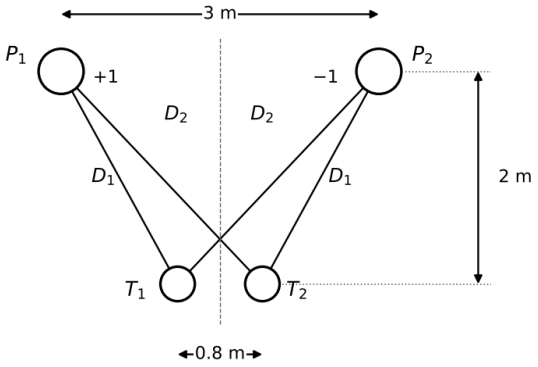


Figure 3: 21-22 1(d): Fig. 1 of the paper (redrawn): figure for Q-1(d)

4.2. Line capacitance:

27 marks, 5 questions, in 2 of 2 papers. Book: Mehta Ch. 9; Grainger Ch. 5.

Most often derivation (3 of 5). Subtopics: Unsymmetrical spacing; Effect of earth.

Formulas:

Subtopic	Formula	Equation	Used in
Unsymmetrical spacing	Capacitance	$C = \frac{q}{V}$	20-21 1(c)
	Field of a line charge	$E = \frac{q}{2\pi\varepsilon_0\, x}$	20-21 1(c)
	Potential difference	$V_{12} = \frac{q}{2\pi\varepsilon_0} \ln \frac{D_2}{D_1}$	20-21 1(c), 21-22 5(d)
	Balanced voltages	$V_{ab} + V_{ac} = 3V_{an}$	20-21 1(c)
	Capacitance to neutral	$C_n = \frac{2\pi\varepsilon_0}{\ln(D_{eq}/r)} = \frac{0.0556}{\ln(D_{eq}/r)}\ \mu\text{F/km}$	20-21 1(c)
	Line charging current	$I_c = 2\pi f\, C_n\, V_{ph}$	20-21 1(c), 21-22 5(b)
	Field of a line charge	$g = \frac{q}{2\pi\varepsilon_0\, x}$	21-22 5(d)

Free shared copy · Nur Mohammad

Subtopic	Formula	Equation	Used in
	Capacitance to neutral	$C_n = \dfrac{2\pi\varepsilon_0}{\ln(D_{eq}/r)}$ F/m	21-22 5(d)
Effect of earth	Single-phase line	$C = \dfrac{\pi\varepsilon_0}{\ln(d/r)}$ F/m	21-22 5(a)
	Effect of the earth	$C = \dfrac{\pi\varepsilon_0}{\ln\left(\dfrac{d}{r}\cdot\dfrac{2h}{\sqrt{4h^2+d^2}}\right)}$	21-22 5(a)

Questions:

No.	Paper	Marks	Type	Question
Unsymmetrical spacing				
1	20-21 1(c)	10	derivation	Derive the expression of Capacitance of a three phase line with unsymmetrical spacing.
2	21-22 5(b)	5	numerical	A three phase 50 Hz transmission line has flat horizontal spacing with 3.5 m between adjacent conductors. The conductors are No. 2/0 hard/drawn seven strand copper (outside conductor diameter= 1.05 cm). The voltage of the line is 110 kV. Find the capacitance to neutral and the charging current per kilometre of line.
3	21-22 5(d)	10	derivation	Derive the expression of capacitance of a three phase line with unsymmetrical spacing.
4	21-22 TT1 7(b)	0	derivation repeats 21-22 5(d)	Derive the expression for the capacitance of a three-phase line with unsymmetrical spacing.
Effect of earth				
5	21-22 5(a)	2	theory	How Earth affect on transmission line capacitance?

4.3. Corona:

8 marks, 3 questions, in 2 of 2 papers. Book: Mehta Ch. 8.

Most often theory (2 of 3). Subtopics: Corona effect; Critical disruptive voltage.

Formulas:

Subtopic	Formula	Equation	Used in
Corona effect	Field near the conductor	$g = \dfrac{V}{x\,\ln(d/r)}$	20-21 2(a), 21-22 1(a)
	Strength of air	$g_0 = 30$ kV/cm peak $= 21.2$ kV/cm r.m.s.	20-21 2(a), 21-22 1(a)
Critical disruptive voltage	Surface field	$g_{max} = \dfrac{V}{r\,\ln(d/r)}$	20-21 4(a), 21-22 1(a)
	Critical disruptive voltage	$V_c = m_0\, g_0\, \delta\, r\, \ln\dfrac{d}{r}$ kV	20-21 4(a), 21-22 1(a)
	Air density factor	$\delta = \dfrac{3.92\,b}{273+t}$	20-21 4(a), 21-22 1(a)
	Visual critical voltage	$V_v = m_v\, g_0\, \delta\, r\left(1+\dfrac{0.3}{\sqrt{\delta r}}\right)\ln\dfrac{d}{r}$	20-21 4(a)

Free shared copy · Nur Mohammad

Questions:

No.	Paper	Marks	Type	Question
Corona effect				
1	20-21 2(a)	1	theory	Define Corona Effect.
Critical disruptive voltage				
2	20-21 4(a)	5	theory	Define critical disruptive voltage. Write down its significance.
3	21-22 1(a)	2	numerical	Define critical disruptive voltage. Write down it's significance.

4.4. Overhead insulators:

48 marks, 7 questions, in 2 of 2 papers. Book: Mehta Ch. 8.

Most often theory (3 of 7). Subtopics: String efficiency; Failure.

Formulas:

Subtopic	Formula	Equation	Used in
String efficiency	**Capacitance ratio**	$K = \dfrac{C_1}{C}$	20-21 4(b), 21-22 3(c)
	Unit voltages	$V_2 = (1+K)V_1,\ V_3 = (1+3K+K^2)V_1$	20-21 4(b)
	General unit	$V_{k+1} = V_k + K\,(V_1 + V_2 + \cdots + V_k)$	20-21 4(b), 21-22 8(a)
	String efficiency	$\eta = \dfrac{V}{n\,V_n} \times 100\ \%$	20-21 4(b), 21-22 3(d)
	Three-unit string	$\eta = \dfrac{3+4K+K^2}{3(1+3K+K^2)}$	20-21 4(b), 21-22 3(d)
	Capacitance grading	$C_2 = C_1(1+K),\ C_3 = C_1(1+3K)$	20-21 4(b)
	Unit voltages	$V_2 = V_1(1+K),\ V_3 = V_2 + K(V_1+V_2)$	21-22 3(c)
	String voltage	$V = V_1 + V_2 + \cdots + V_n$	21-22 3(c)
	K from measurements	$K = \dfrac{V_2}{V_1} - 1$	21-22 5(c)
Failure	Safety factor of an insulator	$\text{SF} = \dfrac{\text{puncture strength}}{\text{flash-over voltage}}$	20-21 5(a), 21-22 3(a)

Questions:

No.	Paper	Marks	Type	Question
String efficiency				
1	20-21 4(b)	10	theory	What is String Efficiency? Discuss the methods of improving String Efficiency.
2	21-22 3(c)	8	numerical	In a 33 kV overhead line, there are three units in the string of insulators. If the capacitance between each insulator pin and earth is 11% of self capacitance of each insulator, find (i) the distribution of voltage over 3 insulators and (ii) String efficiency.
3	21-22 3(d)	10	derivation	Derive the mathematical expression of String efficiency with proper diagram. What will happen if: (i) $K = 0.2$ ($K = \frac{shunt\ capacitance}{self\ capacitance}$) (ii) $K = 0.8$ (iii) the number of disc increases in the string.

Free shared copy · Nur Mohammad

No.	Paper	Marks	Type	Question
4	21-22 5(c)	8	numerical	A 3-phase transmission line is being supported by three-disc insulators. The potentials across top unit (near to the tower) and middle unit are 8 kV and 11 kV, respectively. (i) Draw the equivalent circuit (ii) Calculate the ratio of capacitance between pin and earth to the self-capacitance of each unit (iii) Calculate the line voltage and (iv) Calculate string efficiency.
5	21-22 TT2 8(a)	5	numerical	A string of 5 insulators is connected across a 100 kV line. If the capacitance of each disc to earth is 0.1 of the capacitance of the insulator, calculate (i) the distribution of voltage on the insulator discs and (ii) the string efficiency.
Failure				
6	20-21 5(a)	5	theory	What are the causes of insulation failure?
7	21-22 3(a)	2	theory	How electrical breakdown happen in a pin-type insulator?

4.5. Mechanical design:

17 marks, 3 questions, in 2 of 2 papers. Book: Mehta Ch. 8.

Most often theory (2 of 3). Subtopics: Sag; Supports.

Formulas:

Subtopic	Formula	Equation	Used in
Sag	**Working tension**	$T = \dfrac{\text{ultimate strength}}{\text{safety factor}}$	20-21 5(c)
	Sag, level supports	$S = \dfrac{w\,l^2}{8\,T}$	20-21 5(c), 21-22 4(a)
	Conductor curve	$y = \dfrac{w\,x^2}{2\,T}$	20-21 5(c)
	Height of supports	$h = \text{ground clearance} + S$	20-21 5(c)

Questions:

No.	Paper	Marks	Type	Question
Sag				
1	20-21 5(c)	10	numerical	A 132 KV transmission line has the following data: Weight of the conductor= 680 kg/km, Length of span= 260 m, Ultimate strength= 3100 kg, Safety Factor= 2. Calculate the height above ground at which the conductor should be supported. Ground clearance required is 10 meters.
2	21-22 4(a)	2	theory	What is Stringing charts?
Supports				
3	21-22 3(b)	5	theory	What kind of line supports are used for distribution purposes at low voltages (upto 11 kV)?

Free shared copy · Nur Mohammad

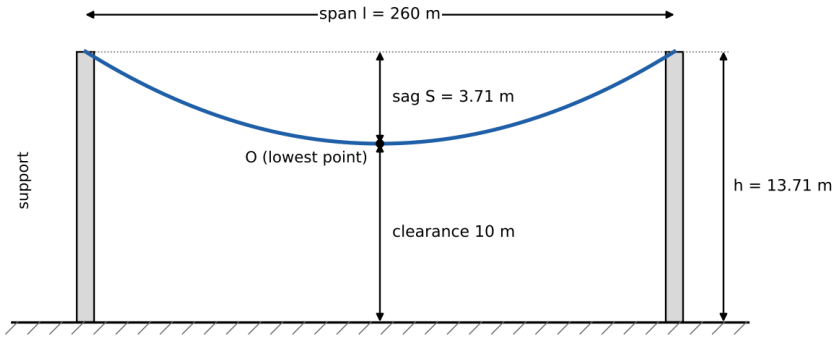


Figure 4: 20-21 5(c): supports at the same level, sag S and clearance

4.6. Underground cables:

85 marks, 11 questions, in 2 of 2 papers. Book: Mehta Ch. 11.

Most often numerical (7 of 11). Subtopics: Dielectric stress; Capacitance; Construction; Grading; Insulation resistance; Economical size.

Formulas:

Subtopic	Formula	Equation	Used in
Dielectric stress	Flux density in the dielectric	$D_x = \dfrac{Q}{2\pi x}$	20-21 3(c)
	Stress from the charge	$g_x = \dfrac{Q}{2\pi\varepsilon_0\varepsilon_r\, x}$	20-21 3(c)
	Core-to-sheath voltage	$V = \dfrac{Q}{2\pi\varepsilon_0\varepsilon_r} \ln\dfrac{D}{d}$	20-21 3(c)
	Dielectric stress	$g_x = \dfrac{V}{x\,\ln(D/d)}$	20-21 3(c)
	Maximum and minimum stress	$g_{max} = \dfrac{2V}{d\,\ln(D/d)},\ g_{min} = \dfrac{2V}{D\,\ln(D/d)}$	20-21 2(d), 21-22 2(c)
	Stress ratio	$\dfrac{g_{max}}{g_{min}} = \dfrac{D}{d}$	20-21 4(c)
	Insulation thickness	$t = \dfrac{D-d}{2}$	20-21 4(c)
	Operating voltage	$V = g_{max}\dfrac{d}{2}\ln\dfrac{D}{d}$	20-21 4(c)
	Cable capacitance	$C = \dfrac{2\pi\varepsilon_0\varepsilon_r}{\ln(D/d)}$ F/m	20-21 3(c), 21-22 2(c)
	Stress in the dielectric	$g = \dfrac{Q}{2\pi\varepsilon_0\varepsilon_r\, x} = \dfrac{V}{x\,\ln(D/d)}$	21-22 2(c)
	Cable charging current	$I_c = 2\pi f C V$	21-22 2(c)
Capacitance	**Belted cable tests**	$C_1 = 3C_s,\ C_2 = C_s + 2C_c$	20-21 3(d)
	Capacitance per phase	$C_N = C_s + 3C_c$	20-21 3(d)

Subtopic	Formula	Equation	Used in
	Cable charging current	$I_c = 2\pi f\, C_N\, V_{ph}$	20-21 3(d)
Grading	Layer stresses	$g_{1max} = \dfrac{Q}{\pi\varepsilon_0\varepsilon_1 d},\ g_{2max} = \dfrac{Q}{\pi\varepsilon_0\varepsilon_2 d_1}$	21-22 4(d)
	Two dielectrics, stresses	$\varepsilon_1 d\, g_{1max} = \varepsilon_2 d_1\, g_{2max}$	21-22 4(d)
	Two dielectrics, voltage	$V = \dfrac{g_{1max}\, d}{2}\ln\dfrac{d_1}{d} + \dfrac{g_{2max}\, d_1}{2}\ln\dfrac{D}{d_1}$	21-22 4(d)
	Capacitance grading	$V = \dfrac{g_{1max}\, d}{2}\ln\dfrac{d_1}{d} + \dfrac{g_{2max}\, d_1}{2}\ln\dfrac{d_2}{d_1} + \dfrac{g_{3max}\, d_2}{2}\ln\dfrac{D}{d_2}$	21-22 2(d)
	Equal maximum stress	$\varepsilon_1 d = \varepsilon_2 d_1 = \varepsilon_3 d_2$	21-22 2(d)
	Graded voltage	$V = \dfrac{g_{max}}{2}\left[d\ln\dfrac{d_1}{d} + d_1\ln\dfrac{d_2}{d_1} + d_2\ln\dfrac{D}{d_2}\right]$	21-22 2(d)
Insulation resistance	**Insulation resistance**	$R = \dfrac{\rho}{2\pi l}\ln\dfrac{r_2}{r_1}$	21-22 4(b)
Economical size	**Most economical size**	$d = \dfrac{2V}{g_{max}},\ D = e\,d = 2.718\,d$	21-22 6(a)

Questions:

No.	Paper	Marks	Type	Question
Dielectric stress				
1	20-21 2(d)	10	numerical	A 33 kV single core cable has a conductor diameter of 1 cm and a sheath of inside diameter 4 cm. Find the maximum and minimum stress in the insulation.
2	20-21 3(c)	10	derivation	Derive the expression of dielectric stress in a single core cable.
3	20-21 4(c)	10	numerical	The maximum and minimum stresses in the dielectric of a single core cable are 40 kV/cm (r.m.s.) and 10 kV/cm (r.m.s.) respectively. If the conductor diameter is 2 cm, find : (i) thickness of insulation (ii) operating voltage
4	21-22 2(c)	8	numerical	A single core cable for use on 11 kV, 50 Hz system has conductor area of 0.645 cm^2 and internal diameter of sheath is 2.18 cm. The permittivity of the dielectric used in the cable is 3.5. Find: (i) the maximum electrostatic stress in the cable, (ii) minimum electrostatic stress in the cable, (iii) capacitance of the cable per km length, and (iv) charging current.
5	21-22 TT2 8(b)	5	numerical repeats 21-22 2(c)	A single core cable for use on 11 kV, 50 Hz system has a conductor area of 0.645 cm^2 and internal diameter of sheath is 2.18 cm. The permittivity of the dielectric used in the cable is 3.5. Find (i) the maximum electrostatic stress in the cable (ii) the minimum electrostatic stress in the cable (iii) the capacitance of the cable per km length (iv) the charging current.
Capacitance				
6	20-21 3(d)	10	numerical	The capacitances of a 3-phase belted cable are $12 \cdot 6\ \mu$F between the three cores bunched together and the lead sheath and $7 \cdot 4\ \mu$F between one core and the other two connected to sheath. Find the charging current drawn by the cable when connected to 66 kV, 50 Hz supply.
Construction				
7	21-22 2(b)	5	theory	Write down the general construction of a 3-conductor cable with required figure.

Free shared copy · Nur Mohammad

No.	Paper	Marks	Type	Question
Grading				
8	21-22 2(d)	10	derivation	Define grading of cables. Why is unequal stress distribution in a cable undesirable? Consider three dielectric layers for capacitance grading and derive the expression of potential difference between core and earthed sheath.
9	21-22 4(d)	10	numerical	A 66 kV single-core lead sheathed cable is graded by using two dielectrics of relative permittivity 5 and 3 respectively; thickness of each being 1 cm. The core diameter is 2 cm. Determine the maximum stress in the two dielectrics.
Insulation resistance				
10	21-22 4(b)	5	numerical	The insulation resistance of a single-core cable is 495 MΩ per km. If the core diameter is 2.5 cm and the resistivity of insulation is $4.5 \times 10^{14}\ \Omega - cm$, find the insulation thickness.
Economical size				
11	21-22 6(a)	2	theory	Find the most economical size of a single-core cable working on a 132 kV, 3-phase system, if a dielectric stress of 60 kV/cm can be allowed.

4.7. Cable faults:

20 marks, 3 questions, in 2 of 2 papers. Book: Mehta Ch. 11.

Most often numerical (3 of 3). Subtopics: Loop tests.

Formulas:

Subtopic	Formula	Equation	Used in
Loop tests	**Varley loop balance**	$\frac{P}{Q} = \frac{R_{loop} - R_X}{R_X + S},\ R_X = \frac{Q\,R_{loop} - P\,S}{P+Q}$	20-21 5(b)
	Equal ratio arms	$R_X = \frac{R_{loop} - S}{2}$	20-21 5(b)
	Murray loop balance	$\frac{P}{Q} = \frac{R_{loop} - R_X}{R_X},\ R_X = \frac{Q}{P+Q} R_{loop}$	21-22 1(b)

Questions:

No.	Paper	Marks	Type	Question
Loop tests				
1	20-21 5(b)	10	numerical	Varley loop test is performed to locate an earth fault on a 20 km long cable. The resistance per km of the single conductor is 20 ohm. The loop is completed with a similar healthy conductor. At balance, the variable resistance connected to the faulty conductor is 200 ohm. The fixed resistors have equal values. Calculate the distance of the fault from the test end.
2	21-22 1(b)	5	numerical	In a test for a fault to earth on a 500 m length of cable having a resistance of 1 Ω per 1000 m, the faulty cable is looped with a sound cable of the same length but having a resistance of 2.25 Ω per 1000 m. The resistance of the other two arms of the testing network at balance are in the ratio of 2.75 : 1. Calculate the distance of the fault from the testing end of the cable.
3	21-22 TT3 9(a)	5	numerical repeats 21-22 1(b)	In a test for a fault to earth on a 500 m length of cable having a resistance of 1 Ω per 1000 m, the faulty cable is looped with a sound cable of the same length but having a resistance of 2.25 Ω per 1000 m. The resistance of the other two arms of the testing network at balance are in the ratio 2.75 : 1. Calculate the distance of the fault from the testing end of the cable.

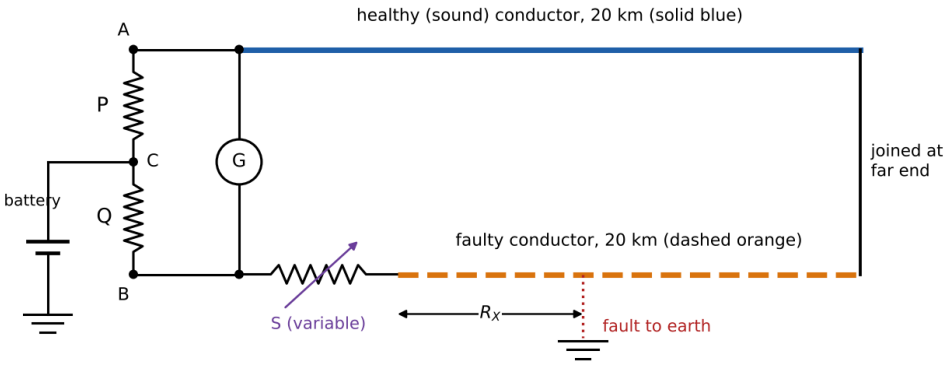


Figure 5: 20-21 5(b): the Varley loop with S in series with the faulty conductor

4.8. Power system stability:

43 marks, 5 questions, in 2 of 2 papers. Book: Grainger Ch. 16.

Most often numerical (4 of 5). Subtopics: Equal area criterion; Transient EMF.

Formulas:

Subtopic	Formula	Equation	Used in
Equal area criterion	**Power-angle equation**	$P_e = \frac{\lvert E\rvert\lvert V\rvert}{X}\sin\delta = P_{max}\sin\delta$	20-21 6(a)
	Swing equation	$M\frac{d^2\delta}{dt^2} = P_m - P_e$	20-21 6(a), 21-22 6(c)
	Equal area criterion	$\int_{\delta_0}^{\delta_{max}} (P_m - P_e)\,d\delta = 0 \;\Leftrightarrow\; A_1 = A_2$	20-21 6(a)
	Critical clearing angle	$\cos\delta_{cr} = \frac{P_m(\delta_{max}-\delta_0) + P_{3max}\cos\delta_{max} - P_{2max}\cos\delta_0}{P_{3max} - P_{2max}}$	20-21 6(a)
	Limit of the swing	$\delta_{max} = 180° - \delta_1$	20-21 6(b)
	Equal area criterion	$A_1 = A_2$	21-22 6(c)
Transient EMF	Terminal voltage angle	$\sin\theta = \frac{P\,X}{\lvert V_t\rvert\lvert V\rvert}$	20-21 6(c)
	Current	$I = \frac{V_t - V}{jX}$	20-21 6(c)
	Transient emf	$E' = V_t + jX'_dI$	20-21 6(c), 21-22 6(d)
	Maximum power	$P_{max} = \frac{\lvert E'\rvert\lvert V\rvert}{X}$	20-21 6(c)
	Transfer reactance (Y to Δ)	$X_{ab} = \frac{X_aX_b + X_bX_c + X_cX_a}{X_c}$	20-21 6(c), 21-22 6(d)
	Power-angle equation	$P_e = \frac{\lvert E'\rvert\lvert V\rvert}{X}\sin\delta = P_{max}\sin\delta$	21-22 6(d)

Questions:

No.	Paper	Marks	Type	Question
Equal area criterion				
1	20-21 6(a)	5	theory	Define Power Angle. Briefly explain Equal Area Criterion.
2	20-21 6(b)	10	numerical	Explain what happens for sudden increase in mechanical input to generator using Pe-δ diagram.
3	21-22 6(c)	8	numerical	Explain what happens for sudden increase in mechanical input to generator using $Pe - \delta$ diagram.
Transient EMF				
4	20-21 6(c)	10	numerical	The generator of Fig. 2 is delivering 1.0 pu power to the infinite bus (|V|=1.0 pu), with the generator terminal voltage (|Vt|=1.0 pu). Calculate the generator emf behind transient reactance. Find the maximum power that can be transferred under the following conditions: (a) System healthy (b) One line shorted (3 phase) in the middle.
5	21-22 6(d)	10	numerical	The generator of Fig. 2 is delivering 1.0 pu power to the infinite bus ($\|V\| = 1.0\ pu$), with the generator terminal voltage ($\|V_t\| = 1.0\ pu$). Calculate the generator emf behind transient reactance. Find the maximum power that can be transferred under the following conditions: (i) System healthy, (ii) One line shorted (3 phase) in the middle and (iii) One line open. Plot all the three power angle curves.

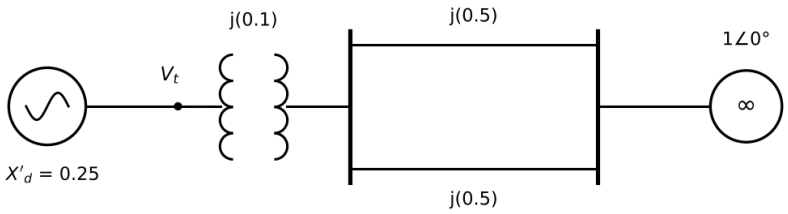


Figure 6: 20-21 6(c): Fig. 2 of the paper (redrawn)

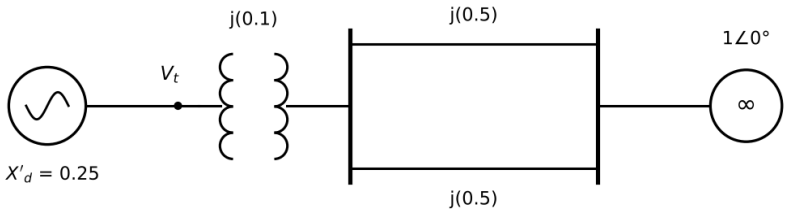


Figure 7: 21-22 6(d): Fig. 2 of the paper (redrawn): figure for Q-6(d)

Free shared copy · Nur Mohammad

4.9. HVDC and FACTS:

11 marks, 3 questions, in 2 of 2 papers. Book: Hingorani and Gyugyi; Rashid Ch. 12.

Most often theory (3 of 3). Subtopics: FACTS; HVDC.

Formulas:

Subtopic	Formula	Equation	Used in
FACTS	**Power over a line**	$P = \frac{V_1 V_2}{X} \sin\delta$	20-21 3(b)
HVDC	Annual cost	$P_1 + P_2 a + \frac{P_3}{a}$	21-22 6(b)
	Kelvin's law	$P_2 a = \frac{P_3}{a}$	21-22 6(b)

Questions:

No.	Paper	Marks	Type	Question
FACTS				
1	20-21 3(b)	4	theory	Describe different FACTS devices and applications.
HVDC				
2	21-22 2(a)	2	theory	What is monopolar link?
3	21-22 6(b)	5	theory	Define HVDC. Discuss the Economics of Power transmission.

5. Derivations:

Every derivation asked, in book order. Each outline gives the steps; the link opens the full working.

No.	Paper	Marks	Derivation	Outline
Line inductance				
1	20-21 2(c)	10	Composite conductors	Write a strand's flux linkage; combine the logarithms; average the strands; read off GMD and GMR.
2	21-22 1(c)	8	Transposition	Write the flux linkage in each section; average; use balanced currents; divide by the current.
3	21-22 4(c)	8	Composite conductors	Write a strand's flux linkage; combine the logarithms; average the strands; read off GMD and GMR.
Line capacitance				
4	20-21 1(c)	10	Unsymmetrical spacing	Write V_ab in each section; average over the cycle; add V_ab and V_ac; use the phase voltage.
5	21-22 5(d)	10	Unsymmetrical spacing	Write V_ab in each section; average over the cycle; add V_ab and V_ac; use the phase voltage.
6	21-22 TT1 7(b)	0	Unsymmetrical spacing	Write V_ab in each section; average over the cycle; add V_ab and V_ac; use the phase voltage.
Overhead insulators				
7	21-22 3(d)	10	String efficiency	Apply KCL at each link; express each unit's voltage by V1; divide V by n times the line unit's voltage.
Underground cables				
8	20-21 3(c)	10	Dielectric stress	Gauss's law gives the flux density; integrate the stress for V; remove Q; read the maximum and minimum.
9	21-22 2(d)	10	Grading	Same charge in each layer; integrate each layer's stress; add the voltages.

Free shared copy · Nur Mohammad

6. Repeat tracker:

Questions that came back, exactly or with new numbers.

Paper	Asked before as	Topic	Subtopic
2021-22 7(b)	2021-22 5(d)	Line capacitance	Unsymmetrical spacing
2021-22 8(b)	2021-22 2(c)	Underground cables	Dielectric stress
2021-22 9(a)	2021-22 1(b)	Cable faults	Loop tests

7. Question style:

How each topic was asked, as a number of questions.

Topic	Theory	Derivation	Numerical
Line inductance	3	3	5
Line capacitance	1	3	1
Corona	2	·	1
Overhead insulators	3	1	3
Mechanical design	2	·	1
Underground cables	2	2	7
Cable faults	·	·	3
Power system stability	1	·	4
HVDC and FACTS	3	·	·

8. Study order:

Topics by marks offered, with the share of all marks covered so far. Papers offer more marks than you answer, so this is a guide to where marks have been, not a score.

No.	Topic	Marks	Covered so far
1	Underground cables	85	26 %
2	Line inductance	66	46 %
3	Overhead insulators	48	61 %
4	Power system stability	43	74 %
5	Line capacitance	27	83 %
6	Cable faults	20	89 %
7	Mechanical design	17	94 %
8	HVDC and FACTS	11	98 %
9	Corona	8	100 %

Free shared copy · Nur Mohammad